

Exam with model answer

Answer the following questions.

Question (1):

[15 Marks]

a) What are the kinds of electrical power generation and the kinds of power stations?

Hydroelectric, Coal fired , Nuclear, Wind power, Diesel electric, Solar, Gasoline engine, Ocean currents

b) Explain the difference between passive and active elements.

Passive elements don't require a power from the supply to produce its effect on a signal. They derive the power of the input signal to perform its action. e.g. Resistor- it doesn't require a separate supply to provide its action of resistance in a circuit. (Also inductors and capacitors.)

In active elements there should be a power source for its working. They require a supply for there working. e.g. transistor - Only after biasing the transistor in required region of operation, its characteristics are applied on the signal. ie, for amplification, transistor require a source from where it can work in. (Also diodes, thyristors and ICs.)

c) The field winding of a DC electromagnet is wound with 960 turns and has a resistance of 30Ω when exciting voltage is 330V, the coil magnetic flux linking is 0.005wb. This winding is connected in series with a capacitor having $C=0.0001F$. Calculate the self-inductance of the coil, the resistance power loss and the energy stored in the magnetic field and the capacitor.

$$N\Phi = I L$$

$$I = V / R = 11 \text{ A}$$

$$\rightarrow L = 0.436 \text{ H}$$

$$P = I^2 R = 3630 \text{ Watt}$$

$$W_L = .5 L I^2 = 26.378 \text{ J}$$

$$W_C = .5 C V^2 = 5.445 \text{ J}$$

Question (2):

[15 Marks]

a) Give proof of the impedance and admittance of long transmission line π connected by parameters from comparison between the general equations and π connection equations.

See in the book

b) State:

1- The corona and the corona critical voltage.

Corona is a phenomenon that has the capability for degrading insulators, and causing systems to fail. Corona critical voltage is the maximum voltage after that the corona happens.

2- The regulation factor.

See in the book

3- The feeder line and distribution line.

The feeder line is the cables between the main power station and substation. Distribution line is the cables between the substation and the customer.


4- The annual cost function.

See in the book

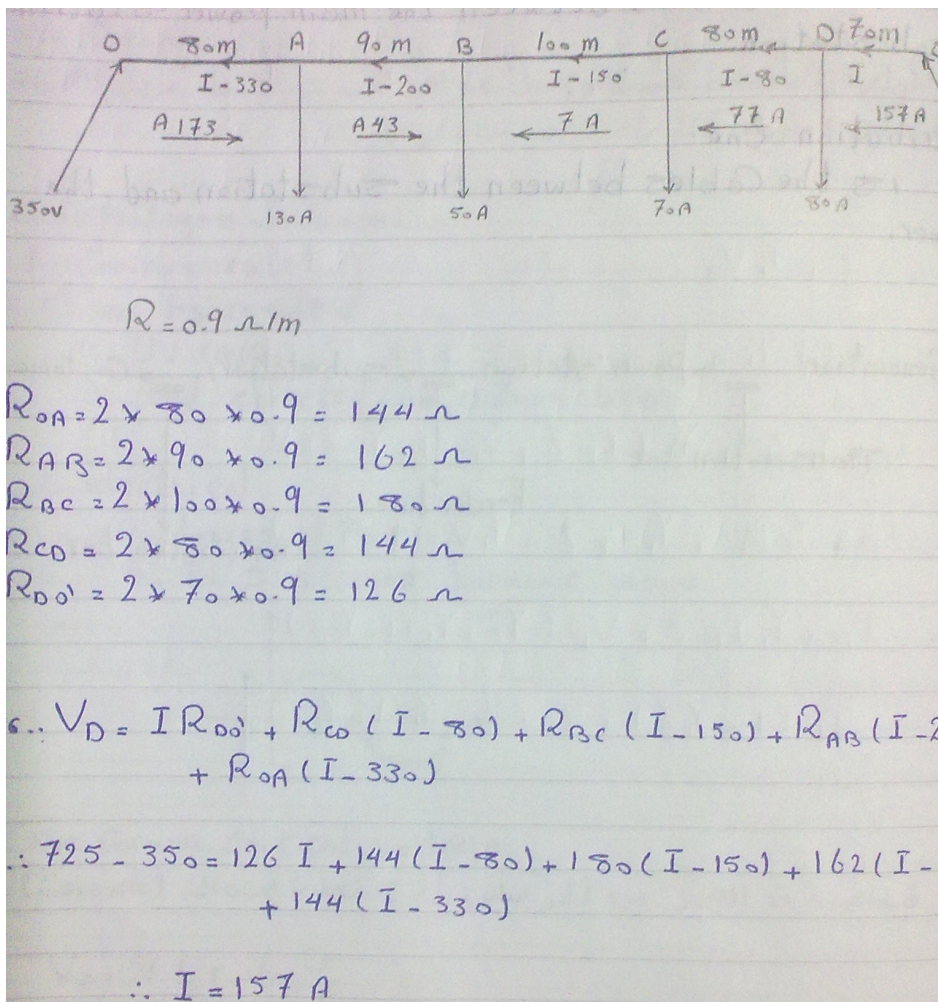Question (3):

[15 Marks]

DC distribution line is fed from two ends. The feeder voltages are 350V and 725V. The resistance per meter is 0.9Ω . The current at each load is $I_1=130A$, $I_2=50A$, $I_3=70A$ and $I_4=80A$. The length of each part is $L_1=80m$, $L_2=90m$, $L_3=100m$, $L_4=80m$ and $L_5=70m$. Calculate the distribution voltage of each point and their efficiency.



$$V_{D_{D_0}} = R_{D_0} \times I_{D_0} = 126 \times 157 = 19782 \text{ V}$$

$$V_{D_{C_0}} = R_{C_0} \times I_{C_0} = 144 \times 77 = 11088 \text{ V}$$

$$V_{D_{B_0}} = R_{B_0} \times I_{B_0} = 180 \times 7 = 1260 \text{ V}$$

$$V_{D_{A_0}} = R_{A_0} \times I_{A_0} = 162 \times -43 = -6966 \text{ V}$$

$$V_{D_{0A}} = R_{0A} \times I_{0A} = 144 \times -173 = -24912 \text{ V}$$

$$\therefore V_D = V_{D_0} - V_{D_{D_0}} = 725 - 19782 = -19057 \text{ V}$$

$$V_C = V_D - V_{D_{C_0}} = -19057 - 11088 = -30145 \text{ V}$$

$$V_B = V_C - V_{D_{B_0}} = -30145 - 1260 = -31405 \text{ V}$$

$$V_A = V_B - V_{D_{A_0}} = -31405 - (-6966) = -24439 \text{ V}$$

$$\therefore \eta = \frac{P_{OIP}}{P_{IIP}}$$

$$P_{IIP} = (725 \times 157) + (350 \times -173) = 53275 \text{ W}$$

$$P_{OIP} = P_{IIP} - P_{Losses}$$


$$P_L = I_{0A}^2 R_{0A} + I_{AB}^2 R_{AB} + I_{BC}^2 R_{BC} + I_{CD}^2 R_{CD} + I_{D0}^2 R_{D0}$$

$$P_L = 8577684$$

$$\therefore \eta = 66.2 \%$$

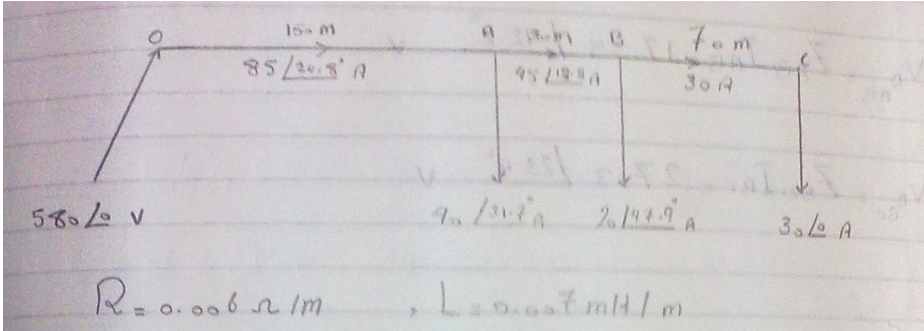Question (4):**[15 Marks]**

AC distribution line, single phase, is fed from one end. The feeder voltage is $580 \angle 0^\circ$ V. The resistance per meter is 0.006Ω , the inductance per meter is 0.007mH and the frequency is 60Hz . The current at each load is $I_1=40\text{A}$ at 0.85 power factor lag, $I_2=20\text{A}$ at 0.67 power factor lag and $I_3=30\text{A}$ at unity power factor. The length of each part is $L_1=150\text{m}$, $L_2=30\text{m}$ and $L_3=70\text{m}$. Calculate the distribution voltage of each point.



$R = 0.006 \Omega / \text{m}$, $L = 0.007 \text{ mH} / \text{m}$

$Z = R + jX_L$

$Z = 0.006 + j(2\pi f L) \Rightarrow Z = 0.006 + j(2\pi \times 60 \times 0.007 \times 10^{-3})$

$\therefore Z = 0.006 + 2.6 \times 10^{-3} j \Omega / \text{m} = 6.5 \times 10^{-3} \angle 23.4^\circ \Omega / \text{m}$

$Z_{OA} = Z \times 2 \times 150 = 1.789 + 0.77 j = 1.95 \angle 23.4^\circ$

$Z_{AB} = Z \times 2 \times 30 = 0.39 \angle 23.4^\circ$

$Z_{BC} = Z \times 2 \times 70 = 0.91 \angle 23.4^\circ$

$V_{D_{OA}} = Z_{OA} \cdot I_{OA} = 165.75 \angle 48.2^\circ \text{ V}$

$V_{D_{AB}} = Z_{AB} \cdot I_{AB} = 17.55 \angle 42.2^\circ \text{ V}$

$V_{D_{BC}} = Z_{BC} \cdot I_{BC} = 27.3 \angle 23.4^\circ \text{ V}$

$\therefore V_A = V_O - V_{D_{OA}} = 580 \angle 0^\circ - 165.75 \angle 48.2^\circ = 485.5 \angle -14.7^\circ \text{ V}$

$V_B = V_A - V_{D_{AB}} = 485.5 \angle -14.7^\circ - 17.55 \angle 42.2^\circ = 475.16 \angle -16.5^\circ \text{ V}$

$V_C = V_B - V_{D_{BC}} = 475.16 \angle -16.5^\circ - 27.3 \angle 23.4^\circ = 455.56 \angle -18.7^\circ \text{ V}$